

A sensor outputs a range of 0.2V to 2.5V as a variable varies over its range.

- Complete the design of the circuit shown in Fig.(1) so that the output voltage varies from 0V to 5V as the output of the sensor varies from 0.2V to 2.5V
- Using hand calculation, determine all nodal voltage for $V_i = 0.1V, 0.2V, 0.5V, 1V, 1.5V, 2V, 2.5V$, and 3V
- Using Pspice, simulate your designed circuit for $V_i = 0.1V, 0.2V, 0.5V, 1V, 1.5V, 2V, 2.5V$, and 3V
- Using LM324 IC shown in Fig.(2), Construct your designed circuit, measure and record all the nodal voltages if $V_i = 0.1V, 0.2V, 0.5V, 1V, 1.5V, 2V, 2.5V$, and 3V
- Write a simple report that includes:
 - Explanation of the function of the circuit of Fig.(1)
 - Indication of all your steps to determine the values of R_x and R_y
 - Simulation circuits and results
 - Comparison of simulation results to hand calculation and practical implementation
 - Conclusion

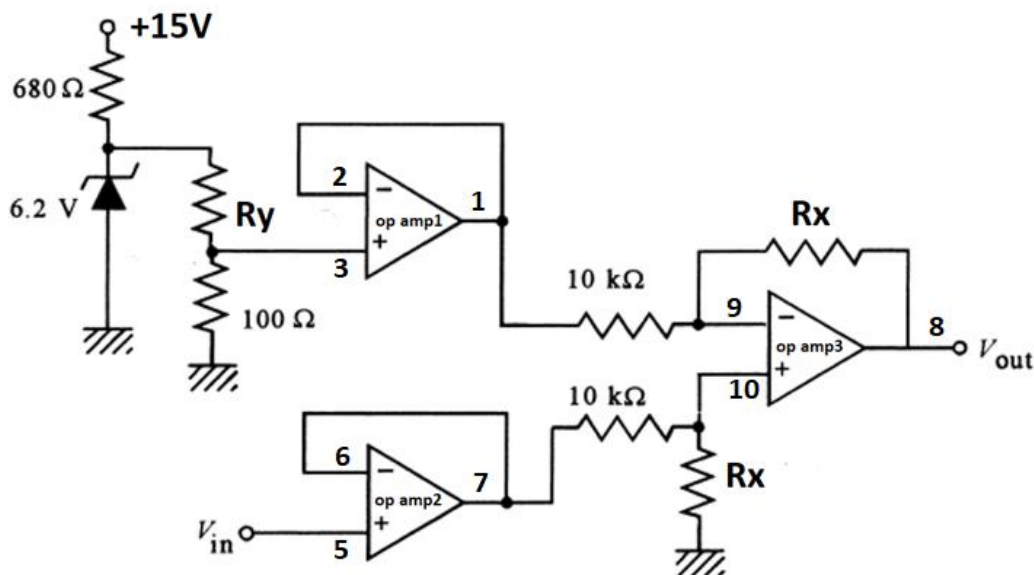


Fig.(1)

LM324 Pinout

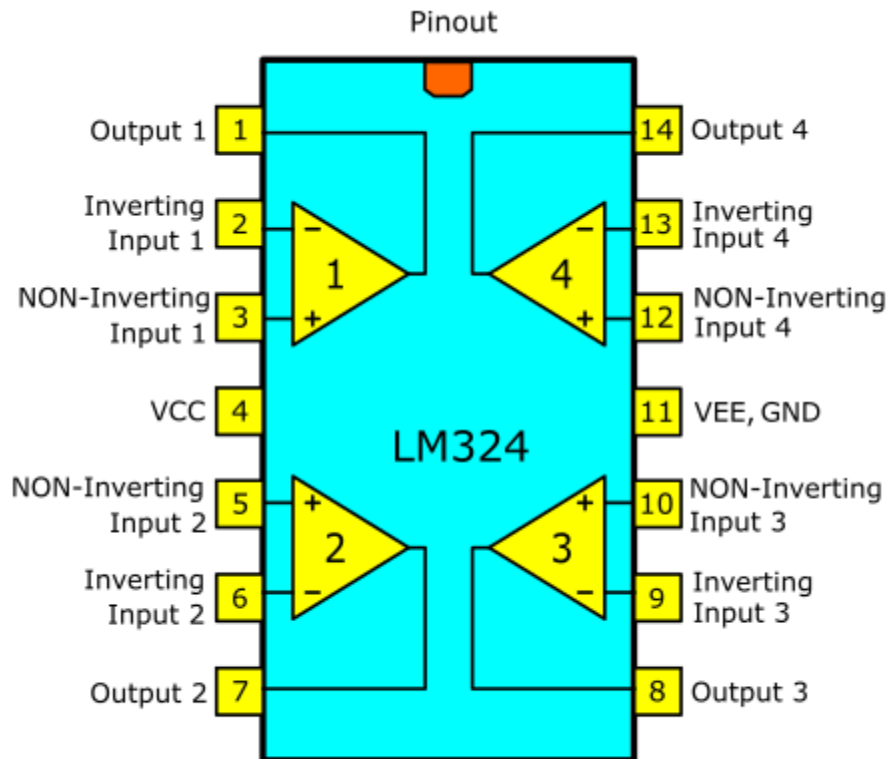


Fig.(2)

Note : VCC = +15V and VEE = - 15V